

## DESIGN AND SIMULATION OF CMOS INVERTER


### AIM :

To design and simulate CMOS Inverting amplifier using Cadence with 180nm technology

### REQUIREMENTS:

EDA Tool: Cadence Virtuoso, Cadence Spectre

### CIRCUIT DIAGRAM:

 

### PROCEDURE :

- **SCHEMATIC ENTRY:** The CMOS circuit will be designed based on the specification and the design will be captured in the Virtuoso Schematic Editor.
- **SIMULATION:** Once the circuit is captured in the Virtuoso Schematic Editor, its functional behavior can be verified using Spectre.

### PHASE I : Schematic entry in Virtuoso Schematic Editor.

1. Workspace creation
  - Make a right click on the Desktop and select the option “Create Folder”
  - Name the folder, for example, we have named it as “inverter”
  - Open the created folder, right click and “Open in terminal”
  - Type the command “csh” to initialize shell and source the cshrc file with the command “source /home/install/cshrc”
2. Invoke Virtuoso
  - Soon after we source the “cshrc” file, we get a display “Welcome to Cadence Tools Suite”.
  - Now invoke virtuoso using the command “virtuoso &” or “virtuoso”
  - We get a virtuoso window as given





11. Supply voltage is added by adding instances of “vdc” from “analoglib” and give appropriate voltages based on specification or technology node.



12. For an input source, “vpulse” is considered and parameters like Voltage 1, Voltage 2, Period, Delay time, Rise time, Fall time and Pulse width



Schematic :

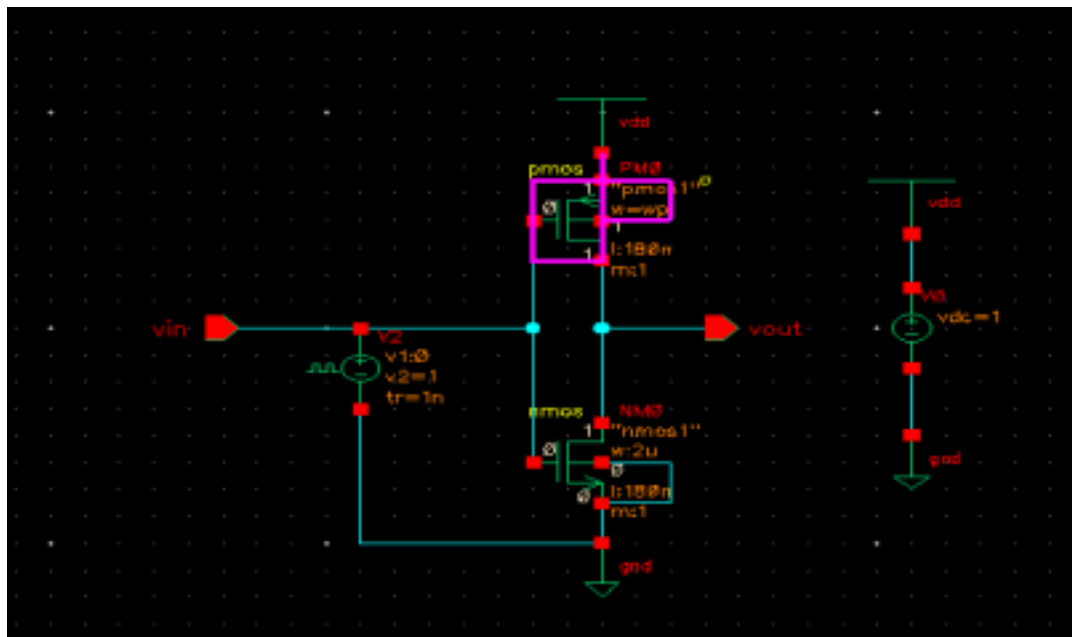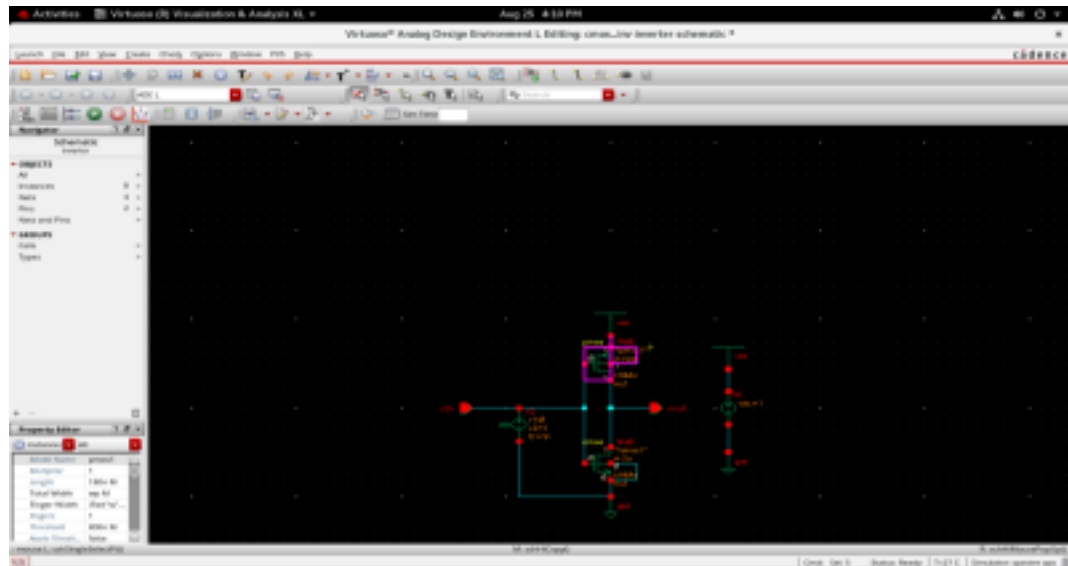

## PHASE II : Functional simulation using Spectre

1. Launch ADE L . make sure Spectre simulator is selected.
2. Model Libraries & Process Corners – to make sure that “.scs” file of the respective technology node has been selected – select “NN”
3. Setup Transient analysis, DC analyses
4. Select outputs to be plotted.
5. To run the simulation, select “Simulation” from ADE L and select the option “Netlist and Run”
6. Input signals and Output signals can be seen separately by selecting “Graph -> Split All Strips”
7. Save the state

**Simulation output :**

