


## DESIGN OF LAYOUT - CMOS INVERTER

### AIM:

To design and simulate CMOS Inverting amplifier using Cadence with 180nm technology

**SOFTWARE:** Cadence Virtuoso, Cadence spectre


### CIRCUIT DIAGRAM:

 

### PROCEDURE:

 
#### 1. Open Existing CMOS Inverter Design.

- Launch Cadence Virtuoso.
- Open the CMOS Inverter design created in Experiment 5 from the Library Manager.


 
#### 2. Modify Power Supply Connections in the Schematic.

- Remove the existing Vdd, GND, and any power supply blocks (marked using yellow square or circle).
- Add ports for Vdd and GND:
  - Go to: **Create > Pin**
  - Add **input/output** pins as needed (set direction to input/output accordingly).
  - Name them as **Vdd** and **GND**.



### 3. Launch the Layout Editor

- In the schematic window, go to the top-left corner:
  - ***Launch > Layout XL***
  - Choose "Create New File" when prompted.
  - Click **OK** to open the new layout view.

### 4. Generate Layout from Schematic.

- In the Layout Editor, go to:
  - ***Connectivity > Generate > All from Source***
- In the dialog box:
  - Set **Distance** to **0.12**
  - Check the box "**In-Boundary**"
  - Click **OK**

### 5. Display Full Layout Details

- Press Shift + F to view the full layout with boundaries and device details.
- To edit transistor properties:
  - Right-click on a **PMOS** or **NMOS** → Select **Properties**
  - Under **Parameters**:
    - Set **Bodytype** to detached (to separate the bulk terminal)
    - Check the **Left Tap** option

### 6. Connect Same Layer Wires

- Press the key **P** to draw paths (wires) between **same layers** (e.g., poly to poly or metal1 to metal1).

### 7. Add Vias (Different Layer Connections)

- To connect **different layers**, use **vias**:
  - Go to: **Create > Via**
  - OR press the shortcut key **O**
  - Choose **Via Type**: e.g., M1-Poly (to connect metal1 to poly layer)

## 8. Access Technology Path (for DRC/LVS)

- In the **Linux file explorer**:
  - Navigate to:  
**Home > Install > Foundry > Analog > 180nm > Ausra-tech-lib**
  - Right-click on the appropriate technology folder → **Properties**
  - **Copy the full path** of the technology file


## 9. Run DRC (Design Rule Check)

- In the layout window, go to:
  - **Asura > Run DRC**
- In the DRC window:
  - Paste the **technology path** copied earlier
  - Set **Technology** to GDK 180
  - Click **Apply** to run DRC and fix any design rule violations

## 10. Run LVS (Layout vs Schematic)

- After successful DRC:
  - Go to: **Asura > Run LVS**
  - Again, paste the **technology path**
  - Set **Technology** to GDK 180
  - Click **Apply**
- LVS will compare the layout with the schematic to ensure both are equivalent.

## LAYOUT OUTPUT:

 

## SUMMARY OF LVS:

