

DESIGN, SIMULATION AND IMPLEMENTATION OF FLIPFLOPS USING ALTERA FPGA

To realize flip flops using Verilog HDL and to perform functional simulation. To synthesize the design and implement using Altera FPGA.


REQUIREMENTS:

EDA Tool: Altera Quartus Prime v17

Hardware: DE1-SoC board

FLIP FLOPS & CHARACTERISTIC EQUATIONS:


JK FLIP

 

TRUTH TABLE

S	R	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

SR FLIP-FLOP

 


TRUTH TABLE

J	K	Q_N	Q_{N+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q_{N+1} = Q_N R' + S R'$$

$$Q_{N+1} = J Q'_N + K' Q_N$$


D-FLIP FLOP

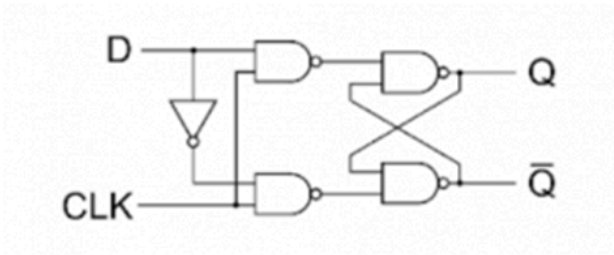

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

$$Q_{N+1} = D$$


T-FLIP FLOP

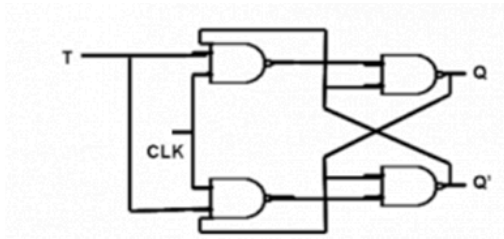


T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

$$Q_{N+1} = Q'_N T + Q_N T'$$


RTL SCHEMATIC:

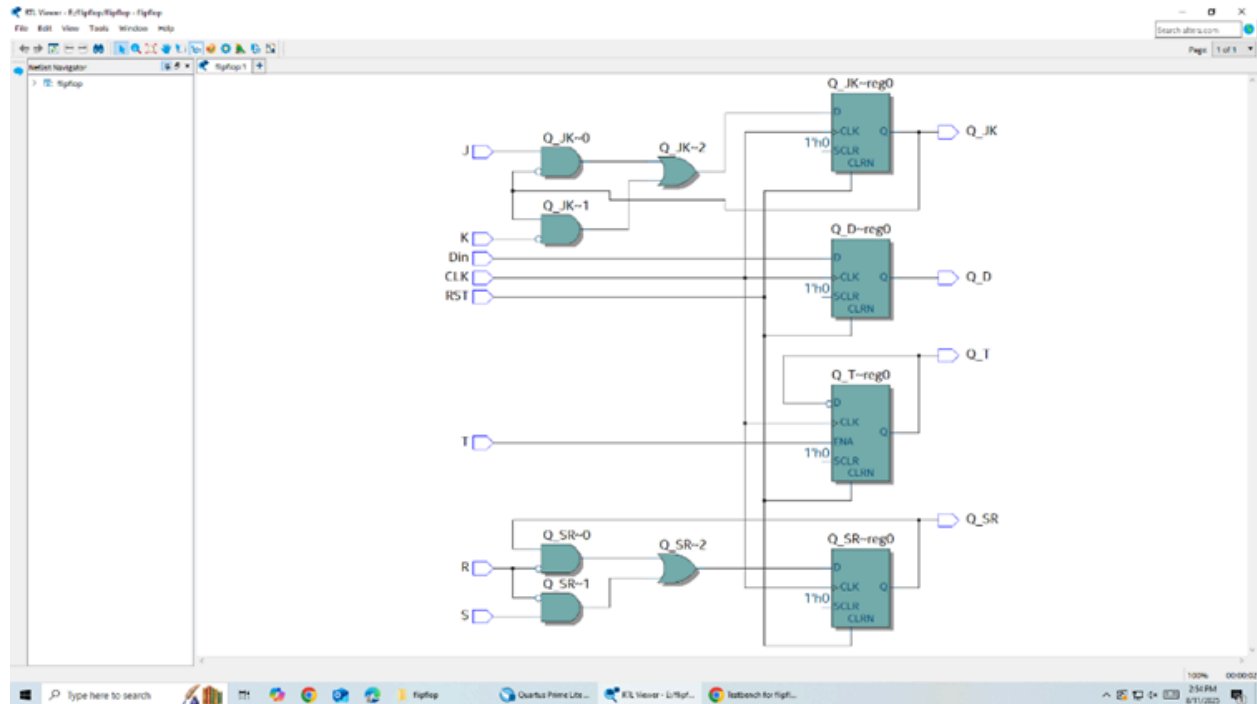

TECHNOLOGY SCHEMATIC:

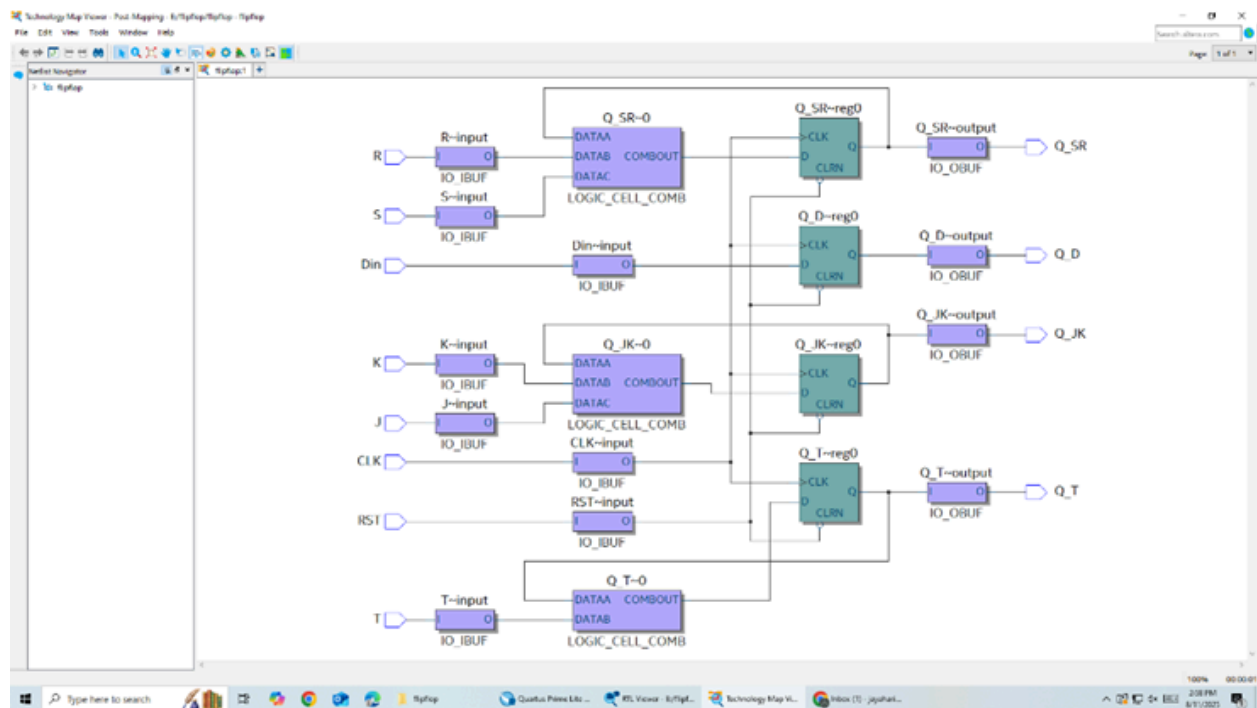

SIMULATION:

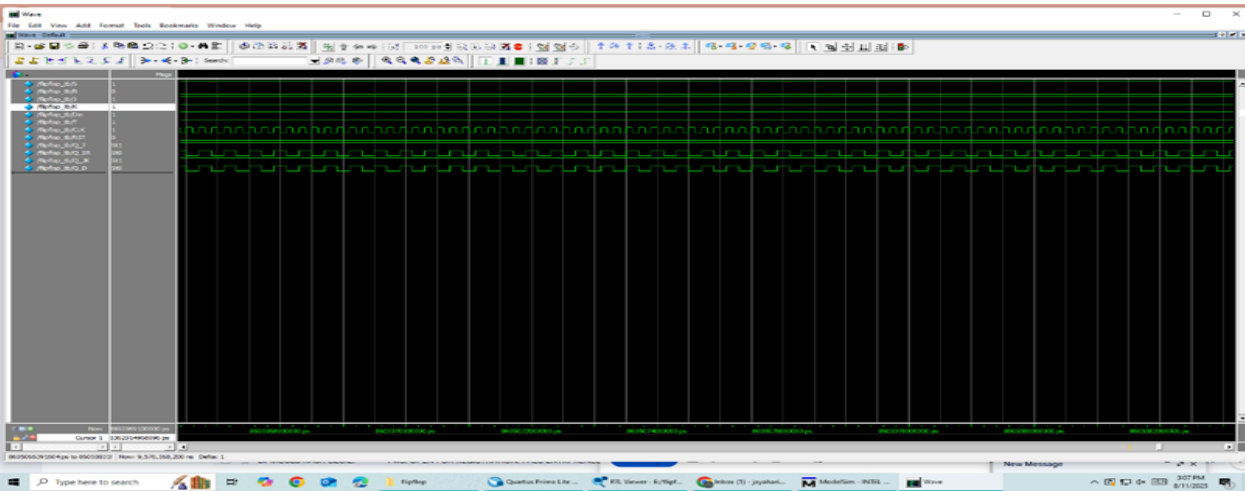

PIN CONFIGURATION & IMPLEMENTATION:

